

## **Laboratory Report 4: Audio Amplifier**

Circuit Theory and Electronics Fundamentals

Department of Electrical and Computer Engineering, Técnico, University of Lisbon

April 22, 2021

Work by:

Beatriz Contente 95772

Francisco Fonseca 95789

Manuel Carvalho 95823


### **Contents**

<b>1</b>	<b>Introduction</b>	<b>2</b>
<b>2</b>	<b>Theoretical Analysis</b>	<b>3</b>
2.1	Gain Stage . . . . .	3
2.2	Output Stage . . . . .	3
<b>3</b>	<b>Simulation Analysis</b>	<b>4</b>
<b>4</b>	<b>Conclusion</b>	<b>5</b>

# 1 Introduction

The objective of this laboratory assignment is to design an audio amplifier circuit, by choosing the architecture of the Gain and Output amplifier stages. The referred circuit is shown in the picture below.

Figure 1: Audio Amplifier Circuit

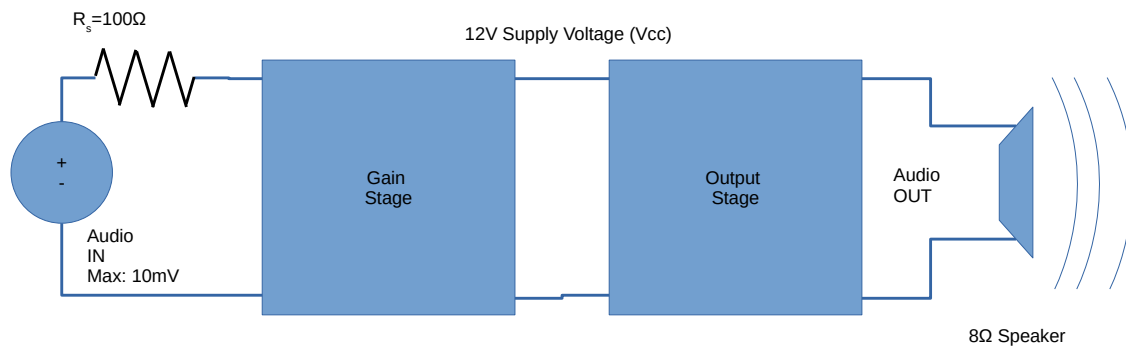

As mentioned above, it is also important to refer that we have developed an optimization algorithm (in Octave) in order to find the number of transistors, the values of the resistors and capacitor that would lead to the best value of merit, computed in Ngspice with the formula given by the Professor.

## 2 Theoretical Analysis

In this section we will discuss the theoretical analysis of our circuit. For this purpose, we will first explain separately the Gain stage and the output stage circuits on the Audio Amplifier circuit. The values used throughout this analysis are shown below.

$V_{ON}$  value is computed using *Ngspice* results for  $V_{out}$ . By definition,  $V_{ON} = \frac{V_{out}}{N_{diodes}}$

Symbol	Value
$R_S$	$100\Omega$
$A_f$	$12V$
$AudioINMax$	$10mV$
$Speaker$	$8\Omega$

Table 1: Values for theoretical analysis

### 2.1 Gain Stage

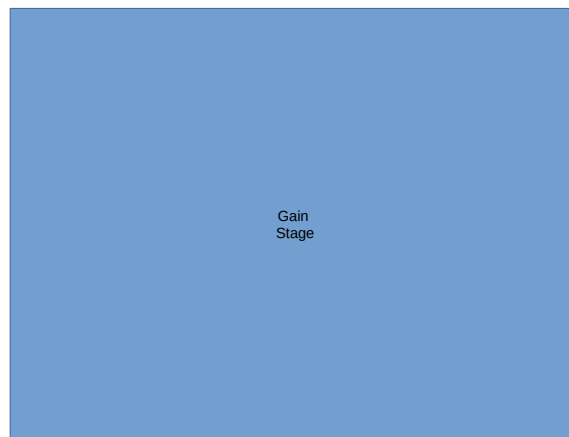


Figure 2: Gain Stage Circuit.

As seen in figure 2...

### 2.2 Output Stage

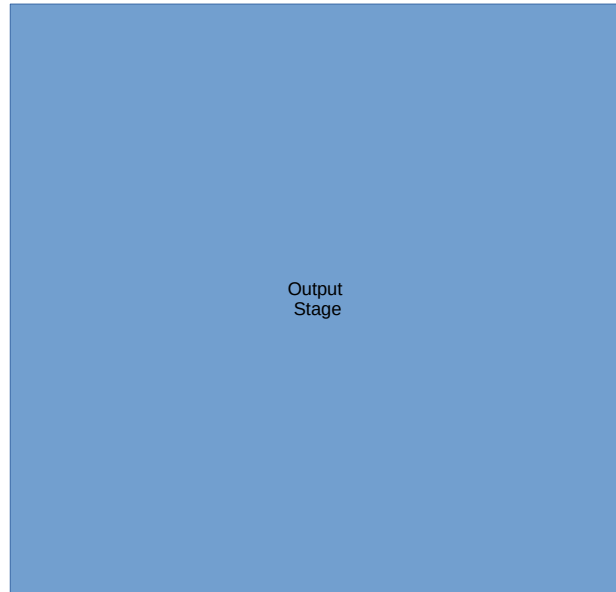


Figure 3: Output Stage Circuit.

### 3 Simulation Analysis

In this section, we will the obtained results by simulating the referred circuit in Ngspice.

## 4 Conclusion